

UNIT-2


LICA

Syllabus ⇒

Op-amp as A.C-amp^r ⇒

- ✓ → Capacitor coupled voltage follower.
- ✓ → High Z_{in} CC Vtg follower.
- ✓ → CC non-inv. amp^r.
- ✓ → High Z_{in} non-inv amp^r.
- ✓ → CC inv. amp^r.
- ✓ → Settling the upper cut-off frequency.
- ✓ → CC difference amp^r.
- ✓ → Use of single polarity power supply.

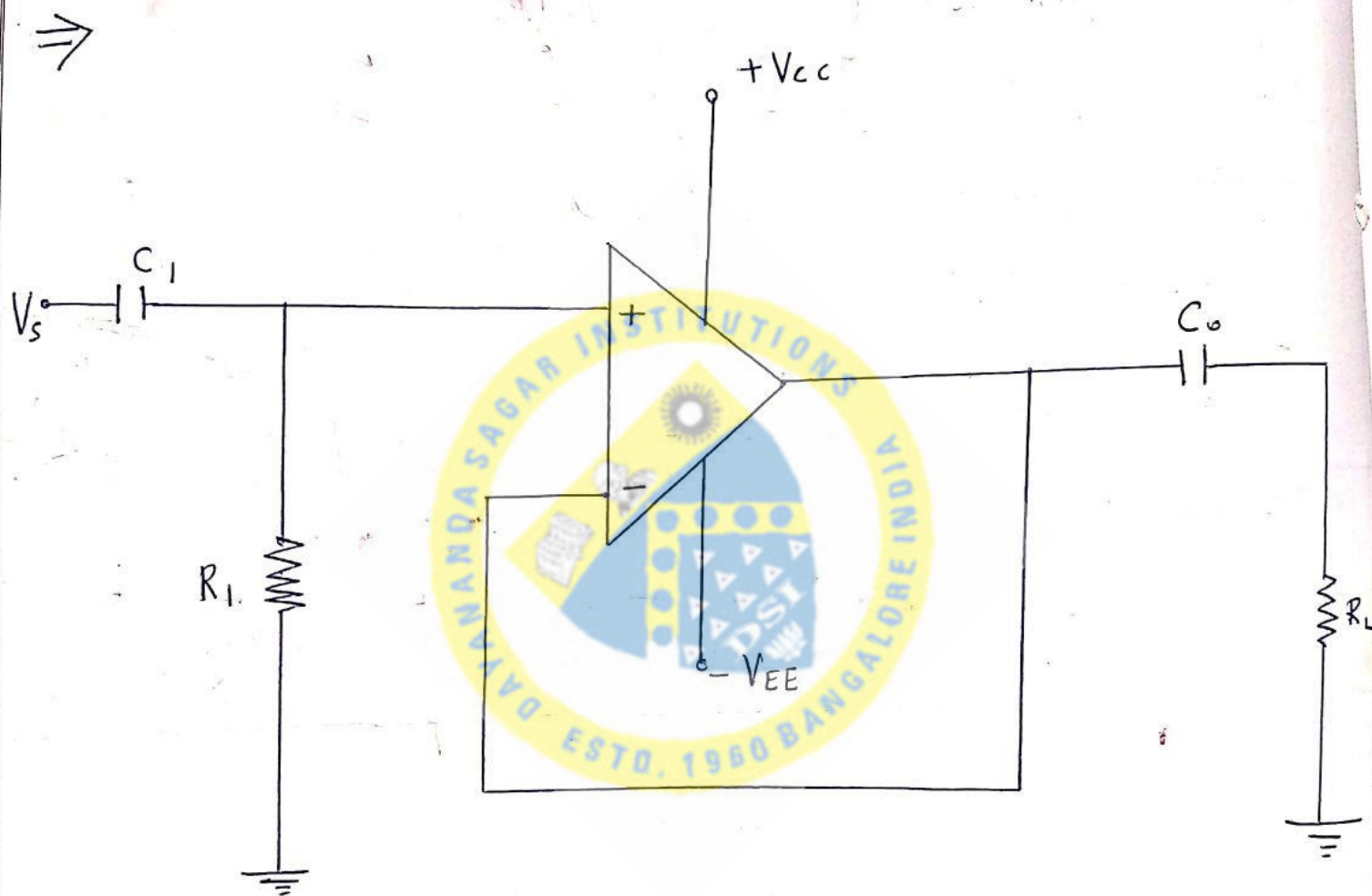
Q.1. With a neat ckt diagram, explain Capacitor-coupled voltage follower with relevant circuit diagram.




- The NON-INV terminal must be grounded via a resistor ' R_1 '.
- This resistor is required to pass the bias current to the amp's NON-INV terminal.
- A resistor equal to ' R_1 ' might be include in series

with the inverting terminal to equalize the $I_B R_B$ voltage and thus minimize the o/p offset voltage.

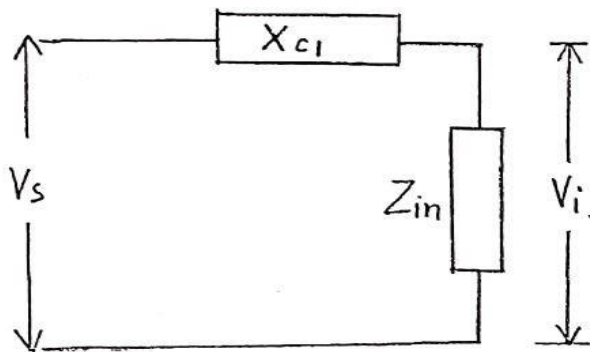→ The output capacitor C_2 blocks the small dc offset voltage.



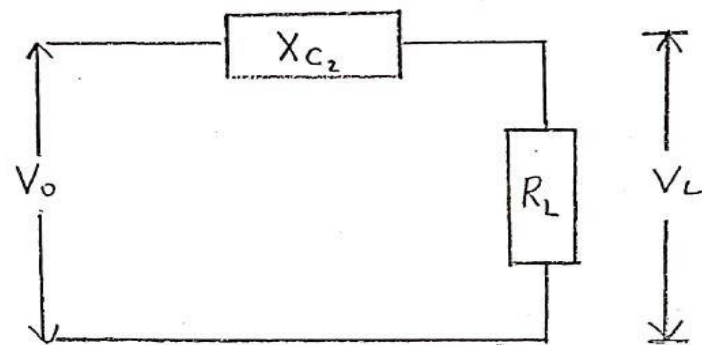(a). The signal v_{tg} is divided across X_{C1} & Z_{in}



(b). The o/p voltage is divided across X_{C2} and R_L .

Design ⇒

→ Design involves calculation of R_1 , C_1 and C_2

→ The maximum value of R_1 is determined as:

$$R_{1(max)} = \frac{0.1 \cdot V_{BE}}{I_{B(max)}}$$

→ Input impedance of the ckt is:

$$Z_{in} = R_1 \parallel Z_i'$$

where, $Z_i' = (1 + M\beta) Z_i$

Z_i' is the i/p impedance at the NON-INV terminal & is very much larger than R_1 .

$$\therefore Z_{in} = R_1$$

→ Load resistor R_L normally has a lower resistance than R_1 .

→ At the lower 3dB frequency ' f_1 ', the impedance of C_1 should be much smaller than Z_{in} .

∴ At f_1 ,

$$X_{C_1} = \frac{Z_{in}}{10}$$

$$\Rightarrow \frac{1}{2\pi f_1 C_1} = \frac{R_1}{10}$$

$$\Rightarrow \boxed{C_1 = \frac{10}{2\pi f_1 R_1}}$$

$$\Rightarrow \boxed{C_1 = \frac{1}{2\pi f_1 \left(\frac{R_1}{10}\right)}}$$

→ The ckt low 3 dB frequency f_1 occur when $X_{C_2} = R_L$

$$\therefore X_{C_2} = R_L \text{ at } f_1$$

$$\Rightarrow \frac{1}{2\pi f_1 C_2} = R_L$$

$$\Rightarrow \boxed{C_2 = \frac{1}{2\pi f_1 R_L}}$$

For LF 353 BIFET →

(1). $R_1 = 1 \text{ M}\Omega$.

(2). $C_1 = \frac{1}{2\pi f_1 \left(\frac{R_1}{10}\right)}$

(3). $C_2 = \frac{1}{2\pi f_1 R_L}$

(4). $Z_{in} = R_1$

Q. 2. With a neat diagram explain High input impedance capacitor coupled voltage follower with relevant design steps and obtain the expression for the input impedance of the circuit.

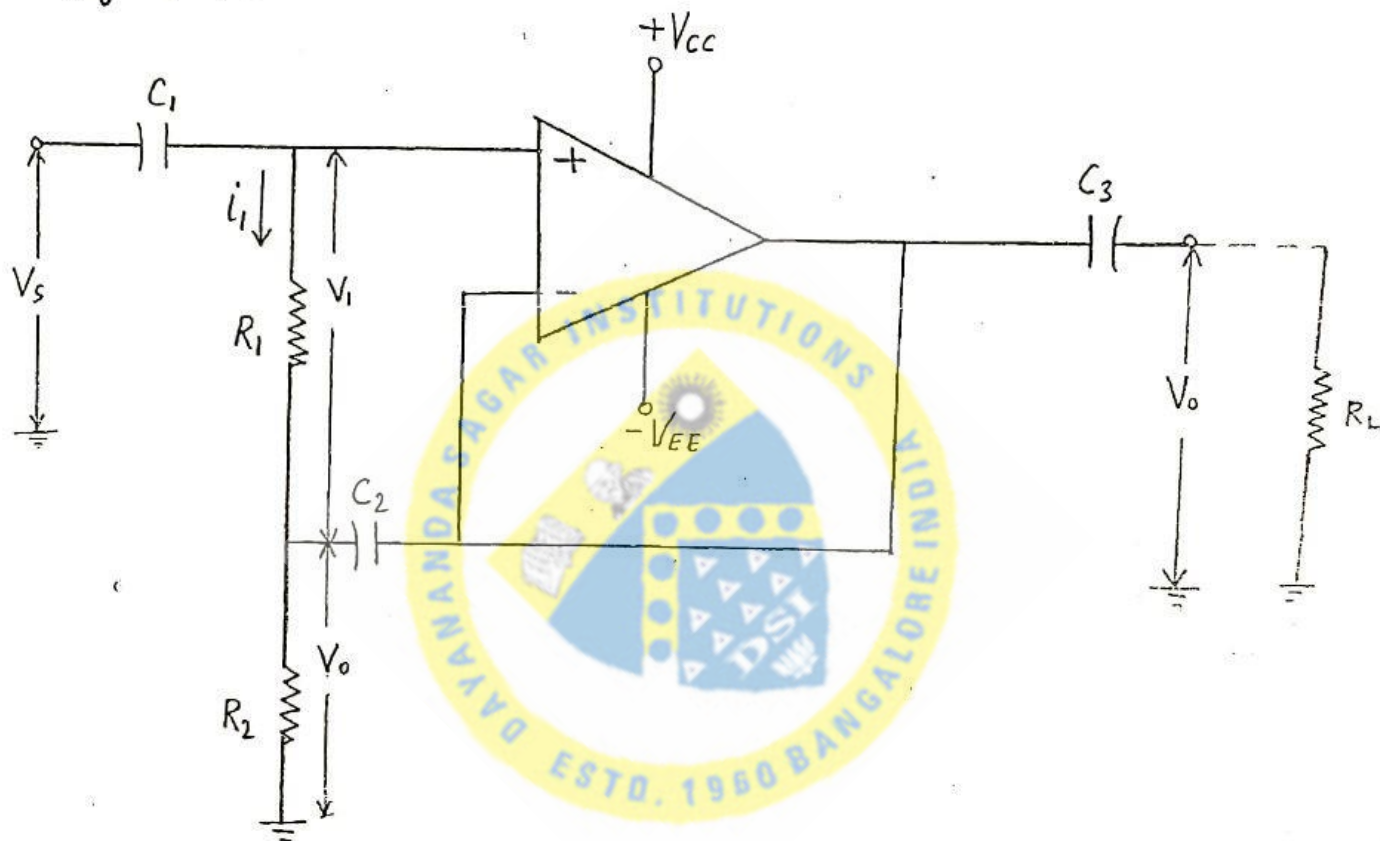


Fig. High input impedance capacitor coupled V.F

- The i/p impedance of the capacitor-coupled voltage follower is set by the value of resistor R_1 . This gives a much smaller i/p impedance than the direct coupled voltage follower.
- Above figure shows a method by which the i/p impedance of the capacitor-coupled v/f follower can be substantially increased.

- Capacitor C_2 couples the circuit o/p v_tg to the junction of resistors R_1 & R_2 .
- C_2 behaves as an ac short circuit. so that V_o is developed across R_2 .
- Applying KVL from source, R_1 & R_2 ,

$$V_s - V_1 - V_o = 0.$$

- The v_tg across R_1 is V_1 & is given by:

$$V_1 = V_s - V_o \quad \text{--- (1)}$$

- WKT open-loop gain is given by $M = \frac{V_o}{V_1}$

$$V_o = M V_1 \quad \text{--- (2)}$$

- Substituting eqn (2) in (1);

$$V_1 = V_s - M V_1$$

$$\Rightarrow M V_1 + V_1 = V_s$$

$$\Rightarrow V_1 (1 + M) = V_s$$

$$\Rightarrow V_1 = \frac{V_s}{1 + M} \quad \text{--- (3)}$$

- The current I_1 is given by:

$$I_1 = \frac{V_1}{R_1} \quad \text{--- (4)}$$

- Substituting eqn (3) in eqn (4), we get:

$$I_1 = \frac{V_s}{(1 + M) R_1} \quad \text{--- (5)}$$

- I/p resistance:

$$Z_{in} = \frac{V_s}{I_1} \quad \text{--- (6)}$$

$$\therefore Z_{in} = \frac{V_s}{\frac{V_s}{(1+M)R_1}}$$

$$\Rightarrow \boxed{Z_{in} = (1+M)R_1} \quad \text{--- (7)}$$

→ Since open loop gain (M) is very high, this modifies the ckt very high I/p impedance.

→ But if stray capacitance b/w the i/p & ground is present, then i/p impedance reduces.

Design steps:

$$(1). R_1(\max) = \frac{0.1 V_{BE}}{I_{B(\max)}}$$

$$(2). R_1 = R_2 = \frac{R_1(\max)}{2}$$

$$(3). C_2 = \frac{1}{2\pi f_1 \left(\frac{R_2}{10} \right)}$$

$$(4). C_1 = C_2$$

$$(5). C_3 = \frac{1}{2\pi f_1 R_L}$$

$$(6). Z_{in} = (1+M)R_1$$

Q. 03. With a neat circuit diagram, explain the operation of a capacitor-coupled Non-inverting amplifier with relevant design steps.

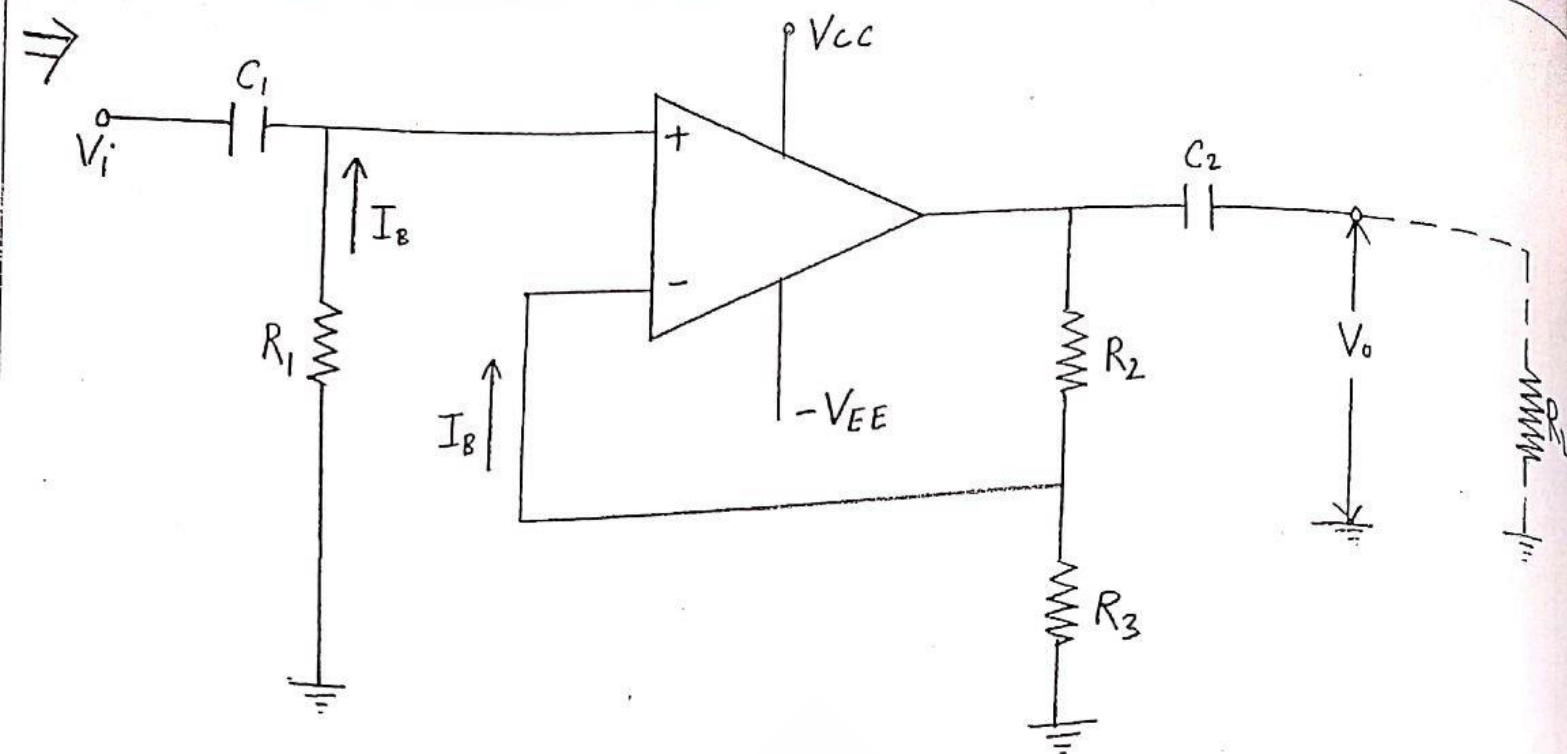


Fig. Capacitor coupled NON-INV amp^r:

- In capacitor-coupled NON-INV amplifier, the NON-INV I/p terminal is grounded via a resistor to provide a path for the i/p bias current.
- The resistor R_1 may be made equal to $R_2 \parallel R_3$ to compensate for the dc offset voltage at the o/p.
- Since the output is also capacitor coupled, it is not of much importance.
- The input impedance is given by $Z_{in} = R_1$.

Design steps:

- (1). $R_1 = R_{1(max)} = \frac{0.1 \cdot V_{BE}}{I_{B(max)}}$
- (2). $X_{C_1} = \frac{R_1}{10} \Rightarrow C_1 = \frac{1}{2\pi f_1 \left(\frac{R_1}{10}\right)}$

$$(3). X_{C2} = R_L \text{ at } f_1$$

$$\therefore C_2 = \frac{1}{2\pi f_1 R_L}$$

$$(4) I_2 = 100 \cdot I_{B \max}$$

$$(5). R_3 = \frac{V_i}{I_2}$$

$$(6). A_v = \frac{V_o}{V_i} \Rightarrow V_o = A_v \cdot V_i$$

$$(7). R_2 + R_3 = \frac{V_o}{I_2} \quad \text{or} \quad A_v = 1 + \frac{R_2}{R_3}$$

$$\Rightarrow R_2 = \frac{V_o}{I_2} - R_3 \Rightarrow R_2 = R_3 (A_v - 1)$$

$$(8). \text{I/p Impedance} \Rightarrow$$

$$Z_{in} = R_1$$

→ The i/p impedance of 100Ω improved by using capacitor C_2 .

→ The voltage is fed back to i/p from the o/p via R_2 , C_2 and R_3 .

→ The feedback factor ' β ' is given by

$$\beta = \frac{R_3}{R_2 + R_3} \quad \text{--- (1)}$$

→ Applying KVL from V_s , R_1 & R_3 , we get

$$V_s - V_i - \beta V_o = 0$$

$$\Rightarrow V_i = V_s - \beta V_o \quad \text{--- (2)}$$

$$\rightarrow M = \frac{V_o}{V_i}$$

$$\Rightarrow V_o = M V_i \quad \text{--- (3)}$$

→ from eqn (2):

$$V_i = V_s - \beta \cdot M \cdot V_i$$

$$\Rightarrow V_i + \beta M V_i = V_s$$

$$\Rightarrow V_i (1 + \beta M) = V_s$$

$$\Rightarrow V_i = \frac{V_s}{1 + \beta M} \quad \text{--- (4)}$$

→ The current $i_i = \frac{V_i}{R_1}$

$$\Rightarrow i_i = \frac{V_s}{(1 + \beta M) R_1} \quad \text{--- (5)}$$

→ Impedance is given by:

$$Z_{in} = \frac{V_s}{i_i} \quad \text{--- (6)}$$

$$\therefore Z_{in} = \frac{\frac{V_s}{V_s}}{(1+\beta M) R_1}$$

$$\Rightarrow \boxed{Z_{in} = (1+\beta M) R_1}$$

Design steps \Rightarrow

$$\textcircled{1}. R_1 + R_3 = R_{1\max}$$

$$R_1 + R_3 = R_{1\max} = \frac{0.1 V_{BE}}{I_{B\max}}$$

$$\textcircled{2} R_1 + R_3 = R_2$$

$$\textcircled{3} R_1 \approx R_2$$

$$\textcircled{4} A_v = 1 + \frac{R_2}{R_3} \Rightarrow R_3 = \frac{R_2}{A_v - 1}$$

$$\textcircled{5} R_1 + R_3 = R_{1\max} \Rightarrow \boxed{R_1 = R_{1\max} - R_3}$$

$$\textcircled{6} X_{C2} = \frac{R_2}{10} \text{ at } f_1$$

$$\therefore C_2 = \frac{1}{2\pi f_1 R_3}$$

$$\textcircled{7} \text{ Choose, } \boxed{C_1 = 1000 \mu F}$$

$$\textcircled{8} X_{C3} = R_L \text{ at } f_1$$

$$C_3 = \frac{1}{2\pi f_1 \left(\frac{R_L}{10}\right)}$$

$\textcircled{9}$ Input impedance:

$$Z_{in} = (1 + M\beta) R_1$$

Design for LF353 \Rightarrow

① Select, $R_2 = 1 \text{ M}\Omega$

② $A_V = \frac{V_o}{V_i}$

$$A_V = 1 + \frac{R_2}{R_3}$$

$$R_3 = \frac{R_2}{A_V - 1}$$

③ $R_1 = R_2 - R_3$

④ $X_{C2} = R_3$ at f_1 ,

$$C_2 = \frac{1}{2\pi f_1 R_3}$$

⑤ $X_{C3} = \frac{R_L}{10}$ at f_1

$$\therefore C_3 = \frac{1}{2\pi f_1 \left(\frac{R_L}{10}\right)}$$

⑥ Choose, $C_1 = 1000 \text{ pF}$

Q5. Draw a neat diagram of a single supply capacitor coupled voltage follower and explaining its operation.

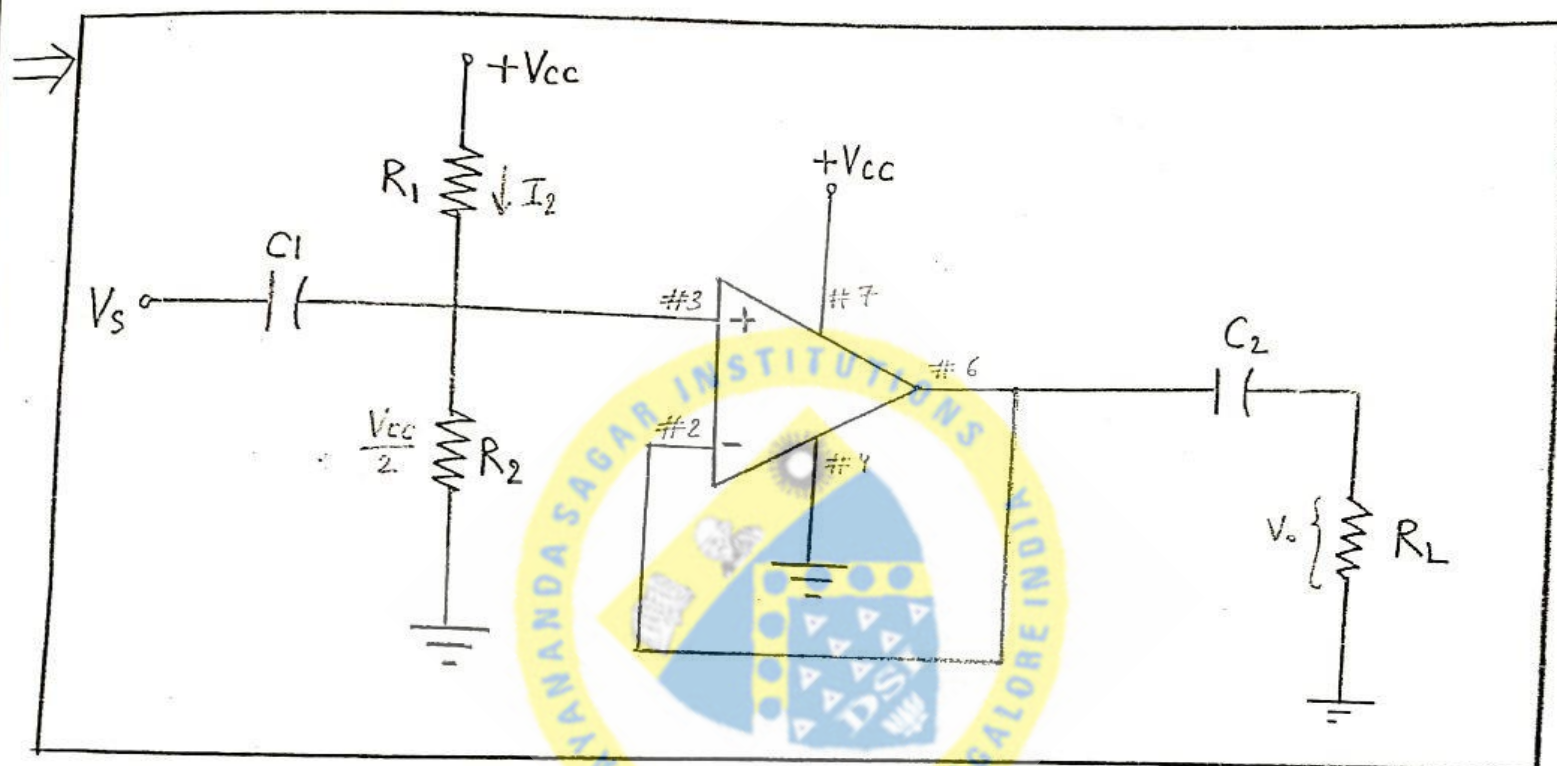


Fig. CC voltage follower using single supply

- A capacitor coupled voltage follower circuit using a single polarity supply is illustrated in above fig.
- The capacitor block the dc bias voltages at the input and the output.
- If the op-amp data-sheet lists the minimum supply voltage as $\pm 9V$, then a minimum of 18V should be used in a single polarity supply.
- The potential divider R_1 & R_2 sets the bias voltage

at the NON-INV i/p terminal as $\frac{V_{CC}}{2}$ i.e. the dc o/p voltage & the INV input are also at $\frac{V_{CC}}{2}$ (\because Voltage follower).

\rightarrow The input impedance of the ckt is $Z_{in} = R_1 \parallel R_2$.

Design steps :

(1). Let, $I_1 = 100 \times I_{B_{max}}$

(2). $R_1 = R_2 = \frac{V_{CC}}{2I_1}$

(3). $Z_{in} = (R_1 \parallel R_2)$

(4). $X_{C_1} = \frac{(R_1 \parallel R_2)}{10} \text{ at } f_1 \Rightarrow C_1 = \frac{1}{2\pi f_1 \left(\frac{R_1 \parallel R_2}{10} \right)}$

(5). $X_{C_2} = R_2 \text{ at } f_1 \Rightarrow C_2 = \frac{1}{2\pi f_1 R_2}$

Q.6 Write the neat diagram of a capacitor coupled inverting amplifier using single polarity supply with design equations.

\Rightarrow The circuit of an inverting amp^r using a single-polarity supply is illustrated in fig. shown below :

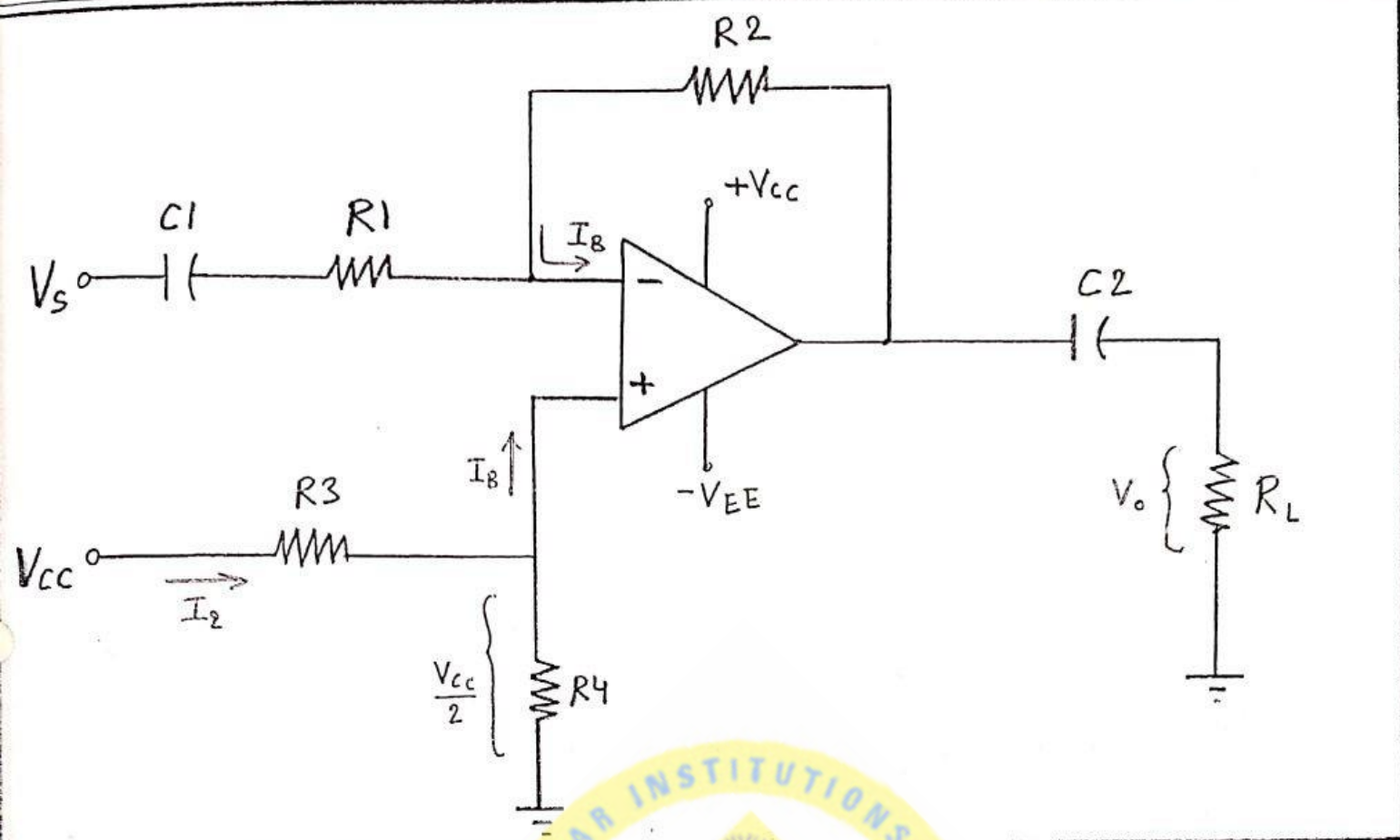


Fig. CC inv. amp^r using a single polarity supply

→ Two resistors R_3 & R_4 form the voltage divider ckt setting the bias voltage to $\frac{V_{cc}}{2}$ at the non-inv. terminal.

→ This makes inv i/p & o/p v_tg equal to $\frac{V_{cc}}{2}$.

Design steps:

(1). Let, $I_1 = I_4 = 100 \times I_{B \max}$.

(2).
$$R_1 = \frac{V_i}{I_1}$$

(3). $A_v = \frac{V_o}{V_i} \Rightarrow V_o = A_v \cdot V_i$

$$\therefore R_2 = \frac{V_o}{I_1}$$

(4). $A_v = \frac{R_2}{R_1} \Rightarrow R_2 = A_v \cdot R_1$

$$(5). \quad R_3 = R_4 = \frac{V_{CC}/2}{I_4}$$

$$(6). \quad C_1 = \frac{1}{2\pi f_1 \left(\frac{R_1}{10} \right)}$$

$$(7). \quad C_2 = \frac{1}{2\pi f_1 R_L}$$

Q.7 *** What is meant by settling upper cut-off in a CC op-amp?

Explain how it is done in an inv. amp.

⇒ → The highest signal frequency that can be processed by an op-amp ckt depends on the op-amp selected (for eg. 741, LF353, etc)

→ for example:

If very low frequency signals are to be amplified, as there would be interference from high frequency noise voltages, since these also get amplified.

→ If these high frequency noise voltages are to be eliminated, there must be a provision for their effective attenuation.

→ This can be achieved by setting the upper cut-off frequency just above the highest desired signal frequency.

→ This can be done by connecting a feedback capacitor C_f from the op-amp o/p to its INV i/p as shown

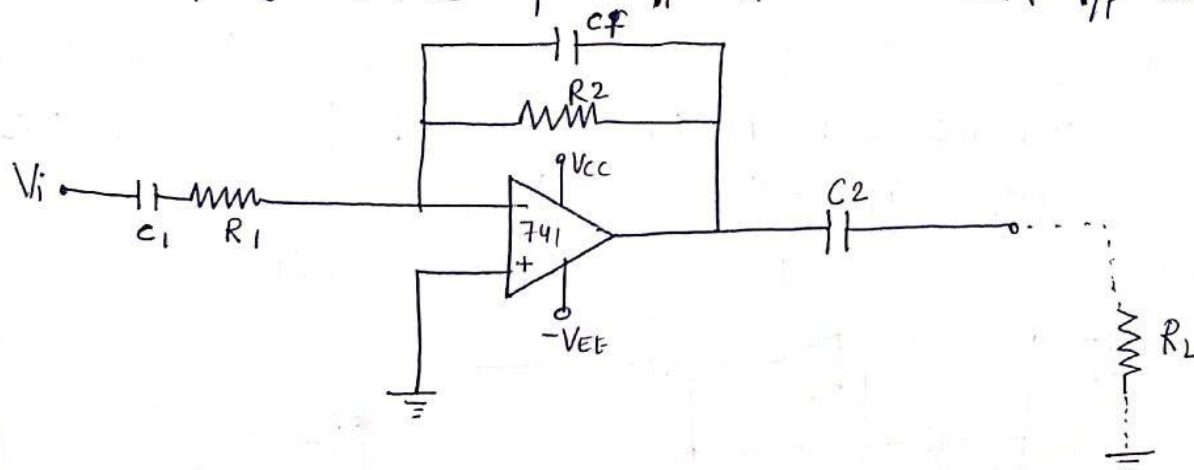


Fig. INV amp^y with feedback capacitor C_f to set the upper cut-off frequency.

$$\begin{aligned}
 A_v &= \frac{R_2 \parallel X_{CF}}{R_1} \\
 &= \frac{R_2 \cdot X_{CF}}{R_1 (R_2 + X_{CF})} \\
 &= \frac{1}{R_1 \left[\frac{R_2}{R_2 \cdot X_{CF}} + \frac{X_{CF}}{R_2 \cdot X_{CF}} \right]} \\
 &= \frac{1}{R_1 \left[\frac{1}{X_{CF}} + \frac{1}{R_2} \right]}
 \end{aligned}$$


Magnitude of A_v :

$$\begin{aligned}
 A_v &= \frac{1}{R_1 \sqrt{\left(\frac{1}{X_{CF}}\right)^2 + \left(\frac{1}{R_2}\right)^2}} \\
 &\quad \text{When, } X_{CF} = R_2 \\
 &= \frac{1}{R_1 \sqrt{\left(\frac{1}{R_2}\right)^2 + \left(\frac{1}{R_2}\right)^2}} \\
 &= \frac{1}{R_1 \sqrt{2 \left(\frac{1}{R_2}\right)^2}} \\
 &= \frac{1}{\frac{R_1}{R_2} \sqrt{2}} \\
 &= \frac{1}{\sqrt{2}} \cdot \left(\frac{R_2}{R_1}\right) \quad \text{--- ①}
 \end{aligned}$$

→ The eqn ① indicates that the gain is 3dB down the normal voltage gain.

→ Thus upper cut-off frequency f_2 (or f_H) for the ckt can be set to the desired frequency f_2 by making $X_{CF} = R_2$ at f_2 .

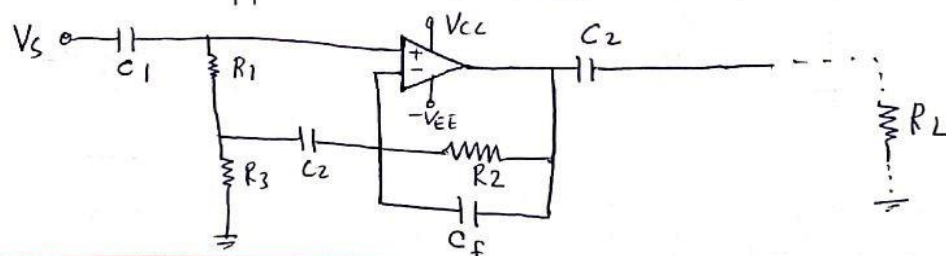→ This is applicable to NON-INV amp^r also.



Numericals :

Q.1. Design High Z_{in} CC-VF using an op-amp having lower cut-off frequency of 50 Hz and \max^m input bias current of 500 nA. The load resistance is 3.9 k Ω . If the open loop gain is 2×10^5 . Find the value of input Z_{in} (consider $M_{min} = 50,000$).

$$\Rightarrow \begin{aligned} f_1 &= 50 \text{ Hz} \\ R_L &= 3.9 \text{ k}\Omega \\ M_{min} &= 50,000 \end{aligned}$$

$$I_{B_{max}} = 500 \text{ nA}$$

$$V_{BE} = 0.7 \text{ V}$$

$$\therefore R_{1_{max}} = \frac{0.1 V_{BE}}{I_{B_{max}}} = 140 \text{ k}\Omega$$


$$R_1 = R_2 = \frac{R_{1_{max}}}{2} = 70 \text{ k}\Omega \quad \text{choose } R_1 = R_2 = 68 \text{ k}\Omega$$

$$C_2 = \frac{1}{2\pi f_1 \left(\frac{R_2}{10}\right)} = 0.5 \mu\text{F} \quad \therefore C_1 = C_2 = 0.5 \mu\text{F}$$

$$C_3 = \frac{1}{2\pi f_1 R_L} = 0.82 \mu\text{F}$$

$$C_3 = 0.82 \mu\text{F}$$
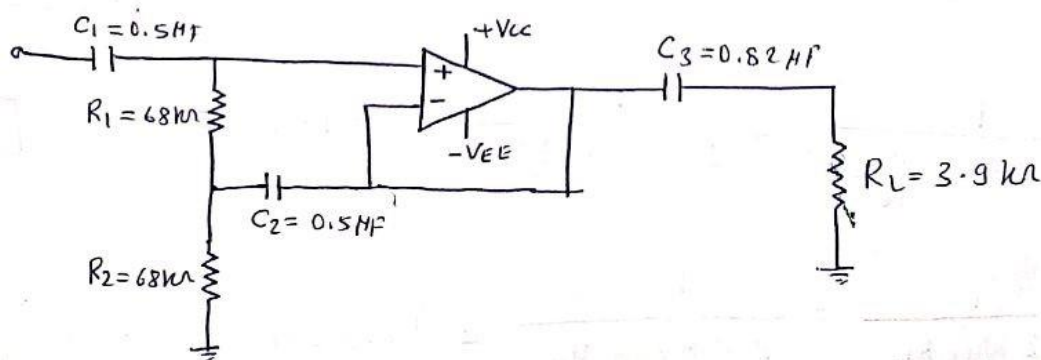
$$\begin{aligned} Z_{in(\min)} &= (1 + M_{min}) R_1 \\ &= (1 + 50000) 68 \text{ k}\Omega \\ &= 3400 \text{ M}\Omega \end{aligned}$$



Q.2. Design a CC-inv amp^r using a IC 741 op. amp to have a voltage gain of 75 output voltage amplifier of 3V and a signal frequency range of 20Hz to 12kHz. The load resistance is 470Ω .

⇒

$$A_v = 75$$

$$V_o = 3V$$

$$R_L = 470\Omega$$

$$f_1 = 20\text{ Hz}$$

$$f_2 = 12\text{ kHz}$$

$$I_{B_{\max}} = 500\text{ nA}$$

$$* \text{ Let, } I_1 = 100 \times I_{B_{\max}}$$

$$\Rightarrow \boxed{I_1 = 50\mu\text{A}}$$

$$* A_v = \frac{V_o}{V_i}$$

$$\Rightarrow V_i = \frac{V_o}{A_v} = \frac{3V}{75}$$

$$\Rightarrow \boxed{V_i = 40\text{ mV}}$$

$$* R_1 = \frac{V_i}{I_1} = \frac{40\text{ mV}}{50\mu\text{A}} = 800\Omega$$

$$\text{Choose } \boxed{R_1 = 820\Omega}$$


$$* A_v = \frac{R_2}{R_1} \Rightarrow R_2 = R_1 \cdot A_v = 820\Omega \times 75 = 61.5\text{ k}\Omega$$

$$\text{Choose. } \boxed{R_2 = 68\text{ k}\Omega}$$

$$* C_1 = \frac{1}{2\pi f_1 \left(\frac{R_1}{10}\right)} = \frac{1}{2\pi \times 20 \times \left(\frac{820}{10}\right)} = 97.5\mu\text{F} \quad \text{Choose } \boxed{C_1 = 100\mu\text{F}}$$

$$* C_2 = \frac{1}{2\pi f_1 R_L} = \frac{1}{2\pi \times 20 \times 470} = 16.93\mu\text{F} \quad \text{Choose } \boxed{C_2 = 18\mu\text{F}}$$
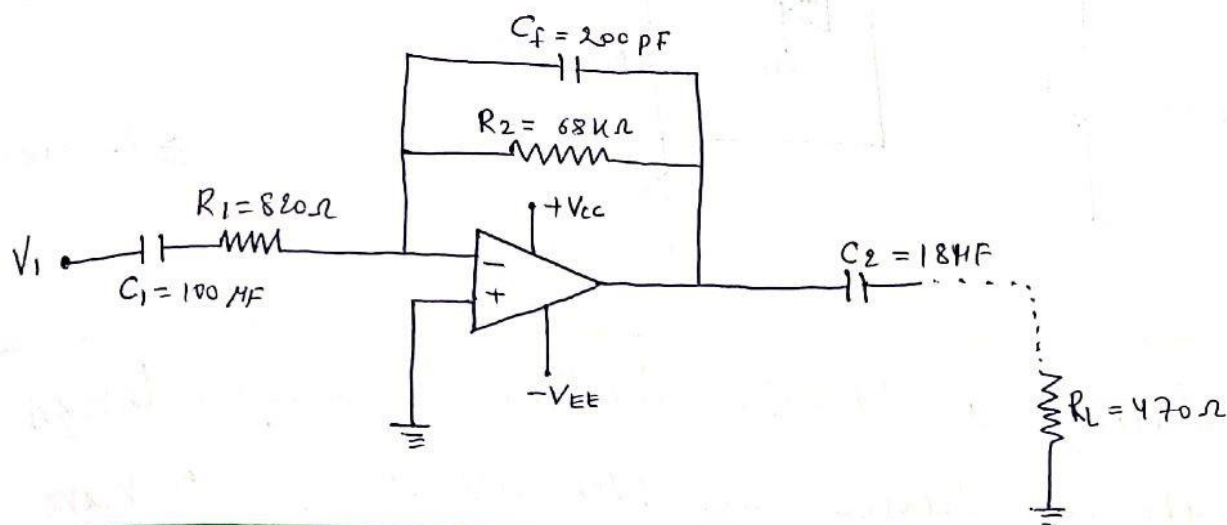
$$C_f = \frac{1}{2\pi f_2 R_2} = \frac{1}{2\pi \times 12 \times 10^3 \times 68 \times 10^3} = 195 \text{ pF} \quad \text{Choose } \boxed{C_f = 200 \text{ pF}}$$



★★ Q.3. A capacitor coupled non-inv op-amp is to have $A_F = 100$ and $V_o = 5V$, $R_L = 10 k\Omega$ and $f_i = 100 \text{ Hz}$. Design suitable ckt.

$$\Rightarrow \begin{aligned} A_F &= 100 \\ V_o &= 5V \\ V_i &= \frac{V_o}{A_F} = \frac{5V}{100} = 50 \text{ mV} \\ R_L &= 10 k\Omega \\ f_i &= 100 \text{ Hz} \end{aligned}$$


$$* R_{1\text{max}} = \frac{0.1 V_{BE}}{I_{B\text{max}}} = 140 k\Omega \quad \text{Choose } \boxed{R_1 = 120 k\Omega}$$

$$* C_1 = \frac{1}{2\pi f_i \left(\frac{R_1}{V_o}\right)} = 0.132 \mu F \quad \text{Choose } \boxed{C_1 = 0.15 \mu F}$$

$$* C_2 = \frac{1}{2\pi f_i R_L} = 0.159 \mu F \quad \text{Choose } \boxed{C_2 = 0.15 \mu F}$$

$$* R_3 = \frac{V_i}{I_2} = \frac{50 \text{ mV}}{50 \mu A} = 1 k\Omega$$
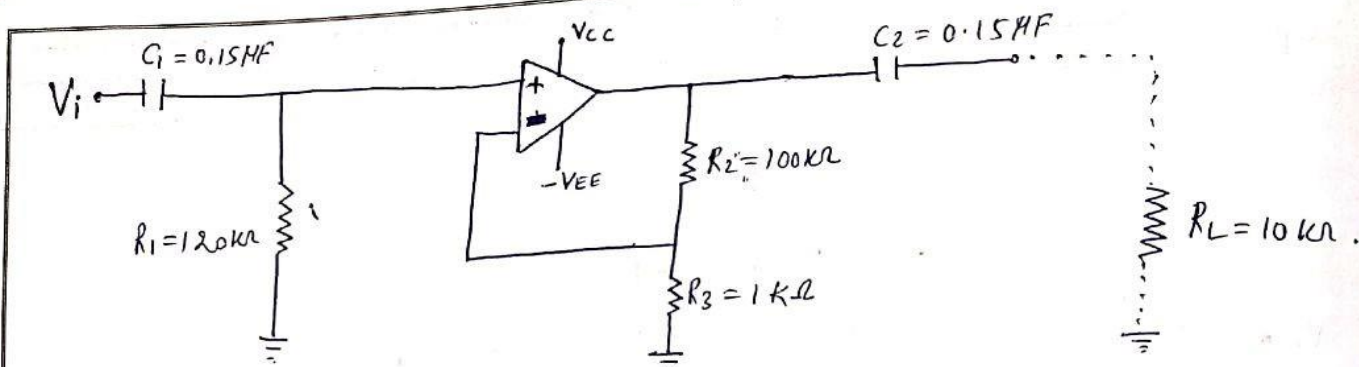
$$* R_2 = \left(\frac{V_o}{I_2} - R_3 \right) = \left(\frac{5V}{50 \mu A} - 1k\Omega \right) = 99 k\Omega \quad \text{Choose } \boxed{R_2 = 100 k\Omega}$$



Q.4. Using a LF353 BIFET op-amp, design a high impedance CC Non-inv amp^r to have a low cut-off frequency of 200 Hz. The i/p & o/p voltages are to be 15 mV and 3V respectively, and minimum load resistance is 12 kΩ.

$$\Rightarrow \begin{aligned} f_1 &= 200 \text{ Hz} \\ V_i &= 15 \text{ mV} \\ V_o &= 3 \text{ V} \\ R_L &= 12 \text{ k}\Omega \\ A_v &= \frac{V_o}{V_i} = \frac{3 \text{ V}}{15 \text{ mV}} = 200 \end{aligned}$$

For BIFET \Rightarrow

Choose: $R_2 = 1 \text{ M}\Omega$

$$R_3 = \frac{R_2}{A_v - 1} = \frac{1 \text{ M}\Omega}{200 - 1} = 5.02 \text{ k}\Omega$$

Choose $R_3 = 4.7 \text{ k}\Omega$

$$R_1 = R_2 - R_3 = 1 \text{ M}\Omega - 4.7 \text{ k}\Omega = 995.3 \text{ k}\Omega$$

Choose $R_1 = 1 \text{ M}\Omega$


Choose $C_1 = 1000 \text{ pF}$

$$C_2 = \frac{1}{2\pi f_1 R_3} = \frac{1}{2\pi \times 200 \times 4.7 \text{ k}} = 0.17 \text{ nF}$$

Choose $C_2 = 0.15 \text{ nF}$

$$C_3 = \frac{1}{2\pi f_l \left(\frac{R_L}{10}\right)} = 0.66 \mu F$$

Choose $C_3 = 0.68 \mu F$

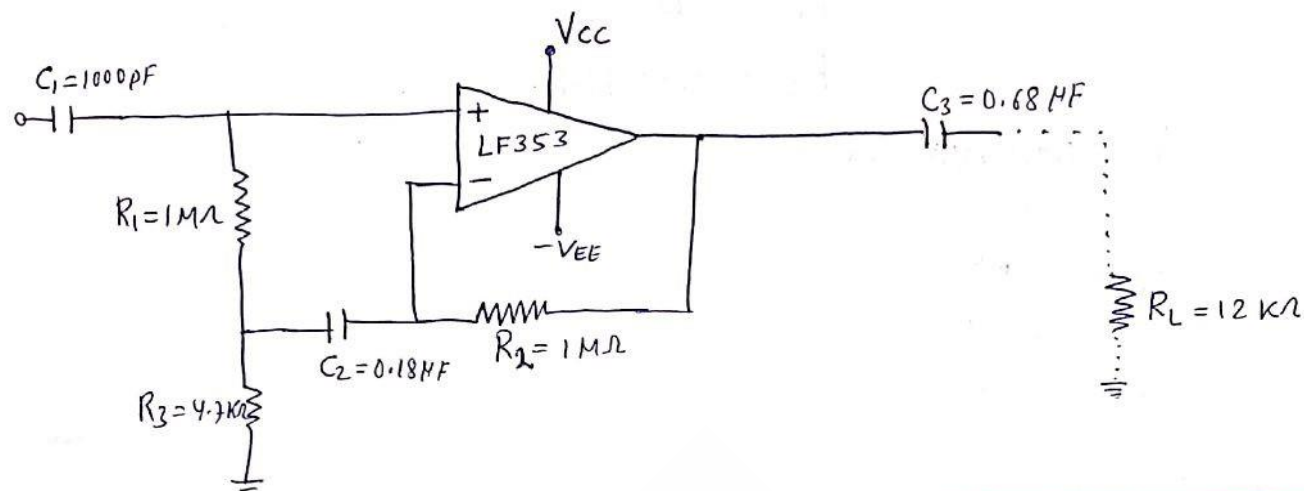

Q.4. Design a BIFET op-amp based high input impedance CC non-inv amp^r for a lower cut-off frequency of 120 Hz. Given : $V_{in} = 20 \text{ mV}$, $V_o = 5 \text{ V}$ and $R_{Lmin} = 10 \text{ k}\Omega$.

⇒ Same as above.

Q.5. Design a high Z_{in} CC - non-inv amp^r to have a cutoff frequency of 200 Hz. The i/p and o/p v_tg are to be 16 mV and 4 V respectively and minimum load resistance is 10 kΩ.

Select $R_2 = 1 \text{ M}\Omega$ and $C_1 = 0.1 \mu F$.

⇒ Same as above.

Q.6 A CC non-inv-amp^r is to have a +24 V supply, a v_tg gain of 100, an output amplitude of 5 V, a lower cutoff frequency of 75 Hz and a minimum load of 5.6 kΩ.

Using 741 op-amp, design a suitable chf

Given $I_{B \max} = 500 \text{ nA}$

$f_1 = 75 \text{ Hz}$

$R_L = 5.6 \text{ k}\Omega$

$\Rightarrow A_v = \cancel{1000} 100$

$V_o = 5 \text{ V}$

$R_L = 5.6 \text{ k}\Omega$

$f_1 = 75 \text{ Hz}$

$I_{B \max} = 500 \text{ nA}$

* $R_1 + R_3 = R_{1 \max} = \frac{0.1 V_{BE}}{I_{B \max}} = \frac{0.1 \times 0.7 \text{ V}}{500 \text{ nA}} = 140 \text{ k}\Omega$

Choose, $R_{1 \max} = 150 \text{ k}\Omega$

* $R_1 + R_3 \approx R_2 = R_{1 \max} \Rightarrow R_2 = 150 \text{ k}\Omega$

* $R_3 = \frac{R_2}{A_v - 1} = \frac{150 \text{ k}\Omega}{100 - 1} = 1.515 \text{ k}\Omega \Rightarrow$ Choose, $R_3 = 1.5 \text{ k}\Omega$

* $R_1 + R_3 = R_{1 \max}$
 $\Rightarrow R_1 = R_{1 \max} - R_3$
 $= 150 \text{ k}\Omega - 1.5 \text{ k}\Omega$
 $= 148.5 \text{ k}\Omega$

Choose $R_1 = 150 \text{ k}\Omega$

* $R_1 \approx R_2 = 150 \text{ k}\Omega$

* $C_2 = \frac{1}{2\pi f_1 R_3} = \frac{1}{2\pi \times 75 \times 1.5 \text{ k}} = 1.41 \text{ nF}$

Choose, $C_2 = 0.15 \text{ nF}$

* Choose $C_1 = 1000 \text{ pF}$

* $C_3 = \frac{1}{2\pi f_1 \left(\frac{R_L}{10}\right)} = \frac{1}{2\pi \times 75 \times \left(\frac{5.6 \text{ k}\Omega}{10}\right)} = 3.789 \text{ nF}$

Choose $C_3 = 3.9 \text{ nF}$

